

The circuit, as described above, is a so-called "Radio Controlled Electronic Switch". It can be used to switch on/off anything electrical, whatever it is. Here are a couple of examples: navigation lights, landing gear, sound systems, glowplug driver, bomb release, parachute, search lights, gyros, and so on. Fig. A shows the regular setup for common accessories such as motors, glowplugs, bomb-doors, relays

Description:

```

R1 = 47K   ICL1 = MC14013B
R2 = 1K    Q1 = BUZ11, IRFZ42, NTE2395, or ECG2395
R3 = 10K   S1 = on/off switch (optional)
          P1 = 100K   C1 = 22nF
          R4 = 10K   Servo lead

```

All resistors 1/4 watt & 5% tolerance, unless otherwise posted.

